

OpAmp

Specification:

$$DC \text{ Gain} = 1000 = 60 \text{ dB}$$

$$GBW = 50 \text{ MHz}$$


$$\text{Phase margin} \approx 60^\circ$$

$$C_L = 1 \text{ pF}, \text{ Skew Rate} = 30 \text{ V}/\mu\text{s}$$

$$\text{Power} = 400 \mu\text{W}$$

$$ICMR (+) = 1.6 \text{ V}$$

$$ICMR (-) = 0.8 \text{ V}$$

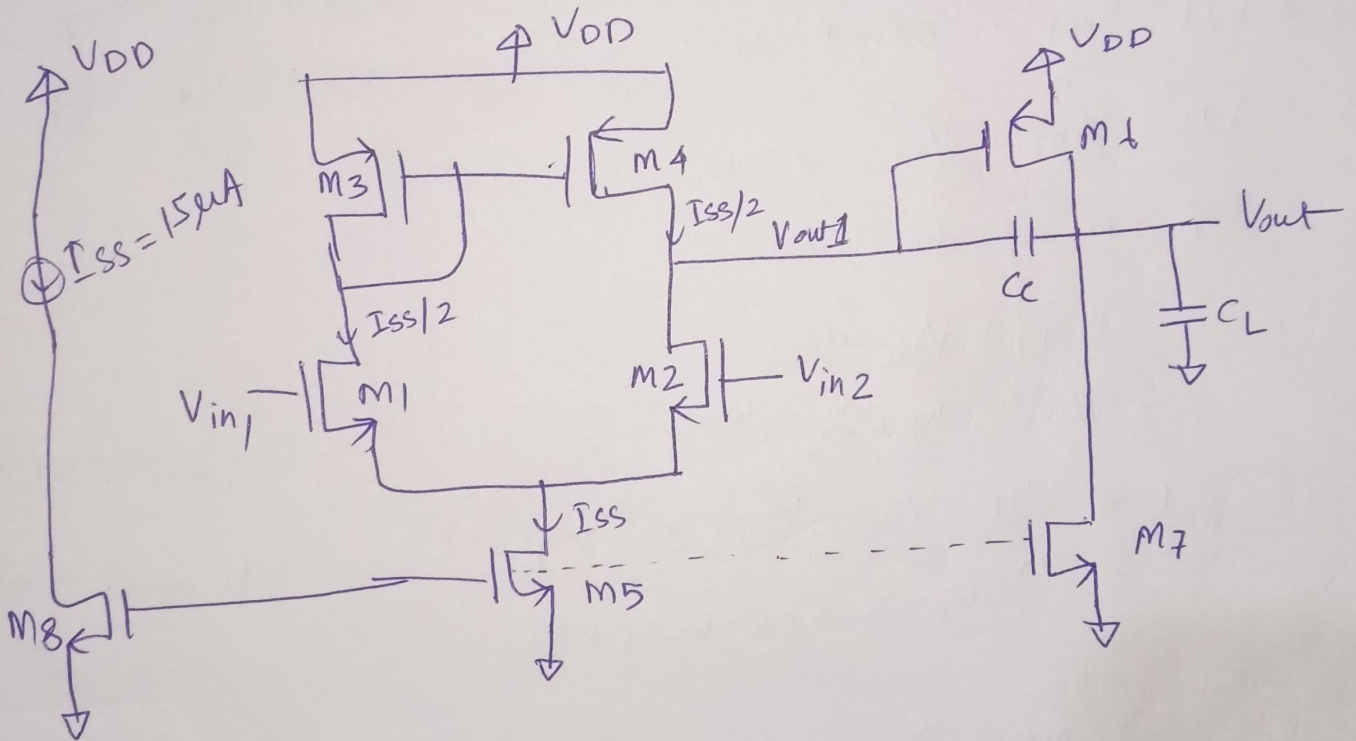

$$L = 500 \text{ nm}$$

$$\Rightarrow C_c \geq 0.22 C_L \Rightarrow C_c \geq 0.22 \times 10^{-12} \text{ F} \Rightarrow \boxed{C_c \geq 220 \text{ fF}}$$

$$\boxed{C_c = 500 \text{ fF}}$$

$$\Rightarrow I_{SS} = C_c SR \Rightarrow I_{SS} = 500 \times 10^{-15} \times 30 \times 10^6 \times 10^{-9} = 15 \times 10^{-6} = \boxed{15 \mu\text{A}}$$

$$\frac{M_1 M_2}{(GBW)} = \frac{g_m}{C_c} \Rightarrow 2\pi \times (GBW) \times C_c = g_m \Rightarrow g_m = 2\pi (50 \times 10^6) \times 500 \times 10^{-19}$$

$$\Rightarrow g_m = 157.142 \mu\text{S}$$

$$\therefore g_{m1} \approx 160 \mu = g_{m2}$$

$$\text{and, } g_{m1} = \sqrt{2\beta I_1} \Rightarrow \frac{g_{m1}^2}{2I_1} = \mu_{\text{cox}} \left(\frac{W}{L}\right)_{1,2}$$

$$\Rightarrow \left(\frac{W}{L}\right)_{1,2} = \frac{160 \times 160 \times 10^{-12}}{15 \times 10^{-6} \times 310 \times 10^{-6}} = 5.505$$

$$\therefore \left(\frac{W}{L}\right)_{1,2} \approx 6$$

M3, M4

$$V_{dd} - V_{in1} = V_{sd3} + V_{dg1}$$

$$V_{dg} = V_{ds} + V_{sg}$$

$$V_{dg} = V_{ds} - V_{gs}$$

$$\therefore V_{dd} - V_{in1} = V_{sd3} + V_{ds1} - V_{gs1}$$

For M1 in saturation:-

$$V_{ds1} \geq V_{gs1} - V_{t1}$$

$$\Rightarrow V_{ds1} - V_{gs1} \geq -V_{t1}$$

$$\text{and } V_{dd} - V_{in1} - V_{sd3} \geq -V_{t1}$$

$$\Rightarrow V_{in1} \leq V_{dd} - V_{sd3} + V_{t1}$$

$$V_{t3 \text{ max}} = 510 \text{ mV}$$

$$V_{t1 \text{ min}} = 470 \text{ mV}$$

$$I_{CMR}(+) = V_{dd} + V_{t1, \text{min}} - \left(V_{t3, \text{max}} + \sqrt{\frac{2I_3}{\mu_p \text{cox} \left(\frac{W}{L}\right)}} \right)$$

$$I_{CMR}(+) = V_{dd} + V_{t1 \text{ min}} - V_{t3 \text{ max}} - \sqrt{\frac{2I_3}{\mu_p \text{cox} \left(\frac{W}{L}\right)}}$$

$$\therefore \sqrt{\frac{2I_3}{\mu_p \text{cox} \left(\frac{W}{L}\right)_{\text{min}}}} = V_{dd} + V_{t1 \text{ min}} - V_{t3 \text{ max}} - I_{CMR}(+)$$

$$= \cancel{4800 \text{ mV}} + \cancel{470}$$

$$\left(\frac{W}{L}\right)_{3 \text{ min}} = \frac{15 \times 10^6}{160 \times 160 \times 60} = 9.765 \Rightarrow \left(\frac{W}{L}\right)_3 \geq 9.765$$

$$\text{So, } \left(\frac{W}{L}\right)_{3,4} \approx 12$$

$$g_{m3} = \sqrt{2 \times \mu_p C_{ox} \left(\frac{W}{L}\right)_3 \times I_{D3}} = \sqrt{15 \times 10^6 \times 60 \times 10^6 \times 12}$$

$$= 10^{-6} \sqrt{15 \times 12 \times 60}$$

$$g_{m3} = 103.92 \mu$$

For M_5, M_8 :-

$$V_{in} = V_{gs1} + V_{ds5}$$

$$V_{ds5} \geq V_{gs5} - V_{t5}$$

$$V_{t1, \max} = 590 \text{ mV}$$

$$V_{in1} - V_{gs1} \geq V_{gs5} - V_{t5}$$

$$V_{in1} \geq V_{gs1} + V_{gs5} - V_{t5}$$

$$ICMR(-) = (V_{gs1} + V_{gs5} - V_{t5})_{\max} = V_{t1, \max} + \sqrt{\frac{I_{ss}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_5}} + V_{t5, \max} + \sqrt{\frac{2 I_{ss}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_5 \min}} - V_{t5, \min}$$

or

$$ICMR(-) = V_{gs1, \max} + \underbrace{(V_{gs5} - V_{t5})_{\max}}_{V_{ds5}} = V_{t1, \max} + \sqrt{\frac{I_{ss}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_5}}$$

$$\therefore V_{ds5} = 800 \text{ m} - 590 \text{ m} - \sqrt{\frac{15 \times 10^{-6}}{310 \times 10^{-6} \times 6}}$$

$$= 210 \text{ m} - 89.8 \text{ m} = 120.2 \text{ m}$$

$$I_{ss} = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_5 (V_{gs} - V_t)^2}{2} \Rightarrow \frac{2 I_{ss}}{\mu_n C_{ox}} = \left(\frac{W}{L}\right)_5 \min \times (V_{gs} - V_t)_{\max}^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_5 \min = \frac{2 \times 15 \times 10^{-6}}{310 \times 10^{-6} \times 6} \times \frac{1}{(V_{ds5})^2} = \frac{30}{310} \times \frac{10^6}{(120.2)^2} = 6.698$$

$$\therefore \left(\frac{W}{L}\right)_5 \geq 6.698 \Rightarrow \left(\frac{W}{8}\right)_{5,8} = 8$$

For m_6

$$g_{m6} > 10g_{m1} \Rightarrow g_{m6} = 10g_{m1} = 1600\mu$$

$$V_{gs,3} = V_{gs,4} \approx V_{gs,6} \Rightarrow \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} = \frac{I_6}{I_4}$$

$$I_p = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right) (V_{gs} - V_t)^2, \quad g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs} - V_t)$$

$$\Rightarrow \frac{g_{m6}}{g_{m4}} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} \Rightarrow \left(\frac{W}{L}\right)_{6,min} = \frac{1600\mu \times 12}{g_{m4}}$$

$$\begin{aligned} \text{and } g_{m4} &= \sqrt{2\beta I} = \sqrt{2 \times \mu_p C_{ox} \left(\frac{W}{L}\right)_4 \times 7.5 \times 10^{-6}} \\ &= \sqrt{15 \times 10^{-6} \times 60 \times 10^{-6} \times 2} = \sqrt{10800 \times 10^{-12}} = 103.9 \times 10^{-6} \end{aligned}$$

$$\therefore \boxed{g_{m4} = 104\mu}$$

$$\Rightarrow \left(\frac{W}{L}\right)_{6,min} = \frac{1600\mu \times 12}{104\mu} = 184.615$$

$$\therefore \boxed{\left(\frac{W}{L}\right)_6 = 190}$$

For m_7

$$\frac{I_6}{I_4} = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} = \frac{190}{12} \Rightarrow I_6 = \frac{190}{12} \times 7.5 \times 10^{-6}$$
$$\therefore \boxed{I_6 = 118.75\mu}$$

$$\frac{I_5}{I_7} = \frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_7} \Rightarrow \frac{15\mu A}{118.75\mu A} = \frac{8}{\left(\frac{W}{L}\right)_7} \Rightarrow \left(\frac{W}{L}\right)_7 = \frac{8 \times 118.75}{15}$$

$$\therefore \left(\frac{W}{L}\right)_7 = 63.33 \Rightarrow \boxed{\left(\frac{W}{L}\right)_7 = 64}$$

$$m_5, m_8 \Rightarrow \frac{4\mu}{0.5\mu}, m_6 = \frac{95\mu}{0.5\mu}$$

$$m_3, m_4 \Rightarrow \frac{6\mu}{0.5\mu}, m_7 = \frac{32\mu}{0.5\mu}$$

$$m_1, m_2 \Rightarrow \frac{3\mu}{0.5\mu}$$

Result 1: $[C_c = 250 \text{ fF}]$

$$BW \approx 53 \text{ MHz} \times$$

$$\text{Gain} \approx 64 \text{ dB} \checkmark$$

$$\theta = -127^\circ$$

$$PM = 53^\circ (\times)$$

Result 2: $[C_c = 230 \text{ fF}]$

$$\theta = -130^\circ, BW = 57 \text{ MHz}, \text{Gain} \approx 64 \text{ dB} \checkmark$$

$$PM = \theta + 180^\circ = 180^\circ - 130^\circ = 50^\circ \times$$

observed, $g_{m1,2} = 117.7\mu \rightarrow \text{Increased to } 146\mu \left[\text{new} \left(\frac{W}{L} \right) = \frac{8.5\mu}{0.5\mu} \right]_{1.2}$

observed $g_{m3,4} = 87.9\mu \rightarrow \text{increased to } 95\mu \rightarrow \text{then gain drastically dropped to } 4.2 \text{ dB.}$

for $m_5, m_7, m_8 \rightarrow \text{increase } L \text{ to } 1\mu\text{m} \rightarrow \text{Gain } \uparrow \text{ by } 3 \text{ dB.}$
 $\left(\frac{W}{L} \right) \text{ same}$ from 65 dB to 68 dB

\rightarrow So, ~~m_6~~ has

$\rightarrow BW \uparrow$

\rightarrow But Phase Margin \downarrow ($\approx 95^\circ$)

So, need to move P_2 to right $\Rightarrow g_{m6}$ has to be \uparrow

$$g_{m6} = \sqrt{2BI}$$

\downarrow
limit reached,

\downarrow
 \rightarrow can not go ~~W~~ beyond 100μ

\rightarrow tried with $L = L_{\min} = 180\text{nm}$

but V_{o6} dropped and gain dropped to 20dB

\rightarrow when,
~~at~~

\rightarrow when, $C_L \rightarrow 15\text{fF}$ from 1pF

$\text{BW} \uparrow$, $\text{PM} \uparrow (\sim 64^\circ)$ ~~***~~

\rightarrow when, $C_c \rightarrow 10\text{fF}$ from 200fF ,

$\text{BW} \uparrow$ to 190MHz , ~~but~~

but $\text{PM} \downarrow (\sim 30^\circ)$